

CNT

Part - 2

$$8 = 2I_1 - 6I_2 + 6I_3 \quad \text{--- (1)}$$

$$I_1 - I_3 = 3A \quad \text{--- (2)}$$

writing KVL at mesh 2

$$-6I_2 + 4(I_3 - I_2) + 2(I_1 - I_2) = 0$$

$$2I_1 - 12I_2 + 4I_3 = 0$$

$$I_1 - 6I_2 + 2I_3 = 0 \quad \text{--- (3)}$$


$$I_1 = 4A$$

$$I_2 = 1A$$

$$I_3 = 1A$$


Example :-

Find the value of current I .

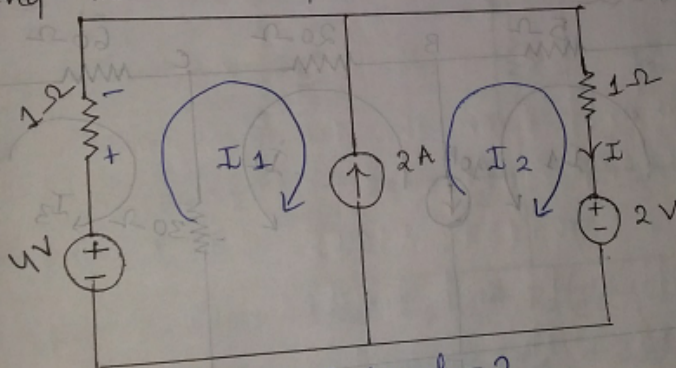


Solution :-

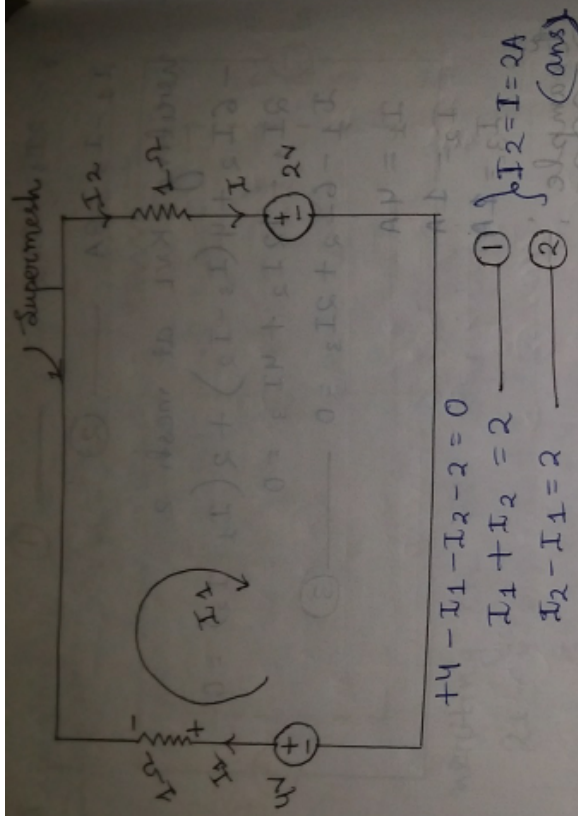- (i) no. of mesh = 2
- (ii) ✓ clockwise direction
- (iii) mesh 1 : $= +4 - I_1$?



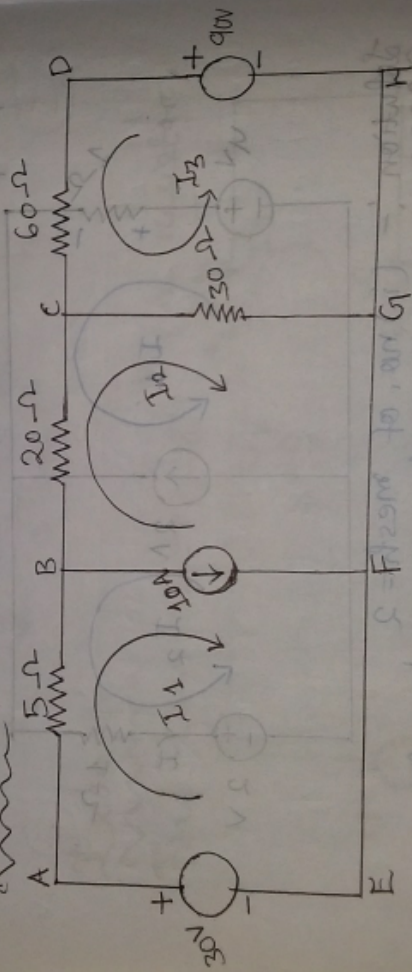Problem: Find current in 20Ω by supermesh method.



Find current in 20Ω by supermesh method.

Solution:

Mesh 1: $30 = 5I_1 + 10 + 20(I_1 - I_2)$

Mesh 2: $10 = 20I_2 + 30(I_2 - I_1)$

Mesh 3: $90 = 60I_3 + 30(I_3 + I_2)$

Mesh 1: $30 = 5I_1 + 10 + 20(I_1 - I_2)$

Mesh 2: $10 = 20I_2 + 30(I_2 - I_1)$

Mesh 3: $90 = 60I_3 + 30(I_3 + I_2)$

Mesh 1: $30 = 5I_1 + 10 + 20(I_1 - I_2)$

$$I_1 - I_2 - 10 = 0$$

$$I_1 - I_2 = 10 \quad \text{--- (2)}$$

$$30 = 5I_1 + 20I_2 + 30(I_2 + I_3)$$

$$30 = 5I_1 + 50I_2 + 30I_3 \quad \text{--- (3)}$$



$$I_1 = 8.889 \text{ A}$$

$$I_2 = -1.11 \text{ A}$$

$$I_3 = -1.37 \text{ A}$$

$$I_{20\Omega} = -1.11 \text{ A}$$


Nodal analysis

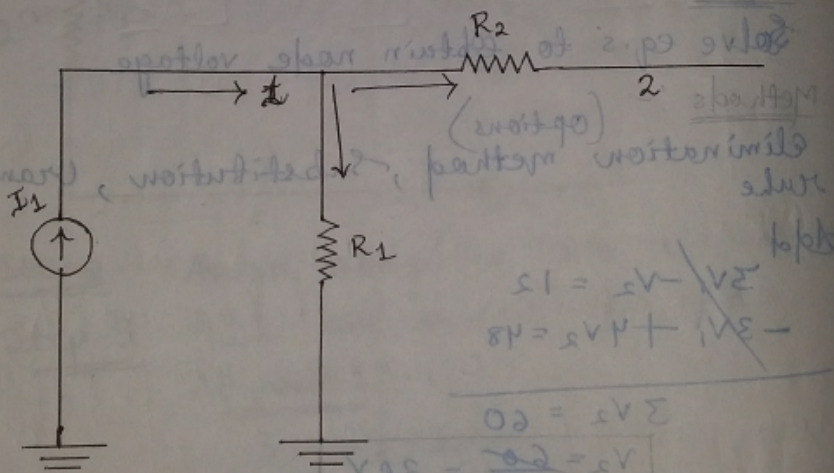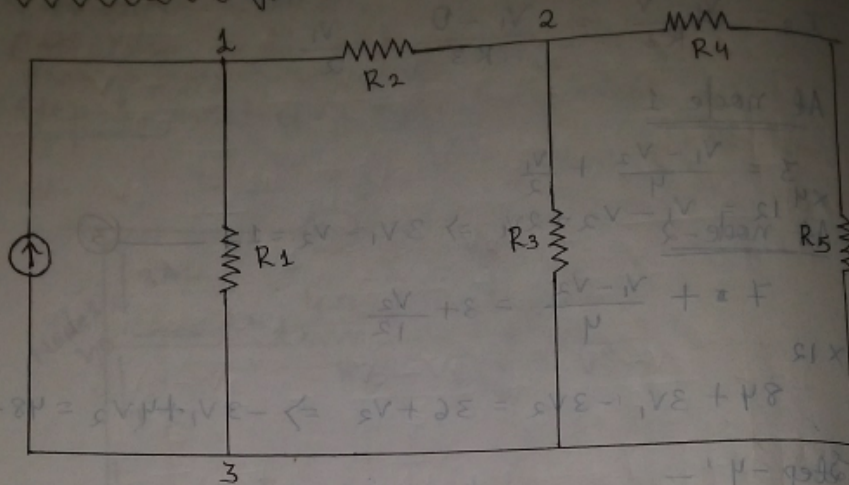

$$I_1 = \frac{V_1}{R_1} + \frac{(V_1 - V_2)}{R_2}$$

where V_1 and V_2 are the voltages at node 1 and 2 respectively.

$$V_1 = 1.66V$$

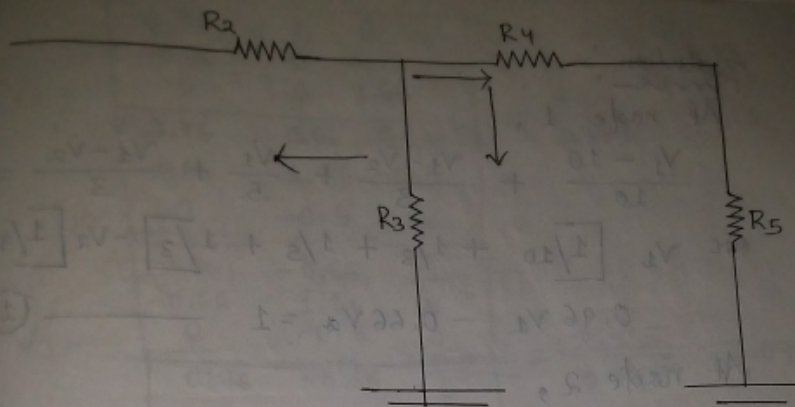

$$(V_2 - V_1) / R_2 + V_2 / R_3 + V_2 / (R_4 + R_5) = 0$$


rearranging the above equations, we have

$$V_1 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - V_2 \left(\frac{1}{R_2} \right) = I_1$$

$$-V_1 \left(\frac{1}{R_2} \right) + V_2 \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{(R_4 + R_5)} \right] = 0$$

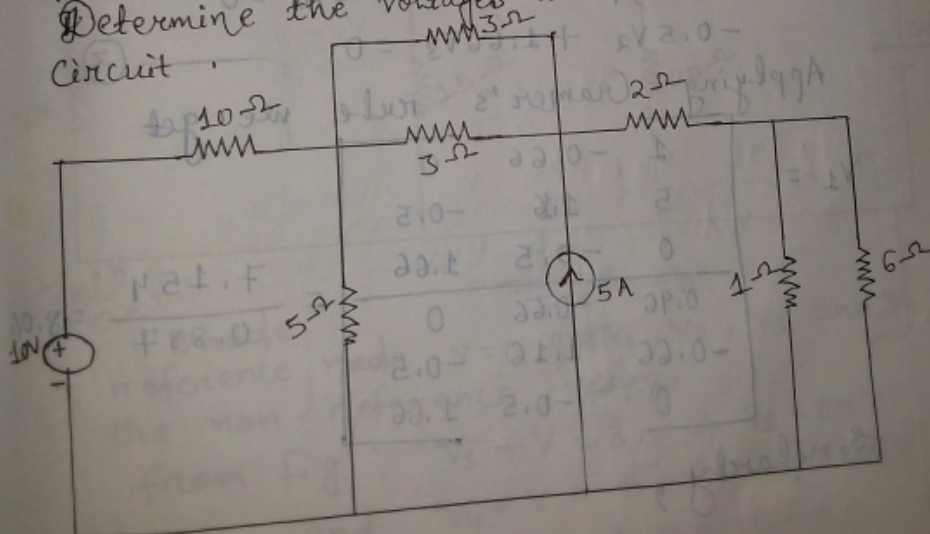Problem :-

Determine the voltages at each node for the circuit.



Solution:-

At node 1,

$$\frac{V_1 - 10}{10} + \frac{V_1 - V_2}{3} + \frac{V_1}{5} + \frac{V_1 - V_2}{3} = 0$$

$$\text{or } V_1 \left[\frac{1}{10} + \frac{1}{3} + \frac{1}{5} + \frac{1}{3} \right] - V_2 \left[\frac{1}{3} + \frac{1}{3} \right] = 1$$

$$0.96 V_1 - 0.66 V_2 = 1 \quad \text{--- (1)}$$

At node 2,

$$0 = \frac{V_2 - V_1}{3} + \frac{V_2 - V_1}{3} + \frac{V_2 - V_3}{2} = 5$$

$$-V_1 \left[\frac{2}{3} \right] + V_2 \left[\frac{1}{3} + \frac{1}{3} + \frac{1}{2} \right] - V_3 \left[\frac{1}{2} \right] = 5$$

$$0 = \left[-0.66 V_1 + 1.16 V_2 - 0.5 V_3 \right] = 5 \quad \text{--- (2)}$$

At node 3

$$\frac{(V_3 - V_2)}{2} + \frac{V_3}{1} + \frac{V_3}{6} = 0$$

$$-0.5 V_2 + 1.66 V_3 = 0 \quad \text{--- (3)}$$

Applying Cramer's rule we get

$$V_1 = \frac{\begin{vmatrix} 1 & -0.66 & 0 \\ 5 & 1.16 & -0.5 \\ 0 & -0.5 & 1.66 \end{vmatrix}}{\begin{vmatrix} 0.96 & -0.66 & 0 \\ -0.66 & 1.16 & -0.5 \\ 0 & -0.5 & 1.66 \end{vmatrix}} = \frac{7.154}{0.887} = 8.06$$


Similarly,

$$V_2 = \begin{bmatrix} 0.96 & 1 & 0 \\ -0.66 & 5 & -0.5 \\ 0 & 0 & 1.66 \end{bmatrix} = \frac{9.06}{0.887} = 10.2$$

$$V_3 = \begin{bmatrix} 0.96 & -0.66 & 1 \\ -0.66 & 1.16 & 5 \\ 0 & -0.5 & 0 \end{bmatrix} = \frac{2.73}{0.887} = 3.07$$

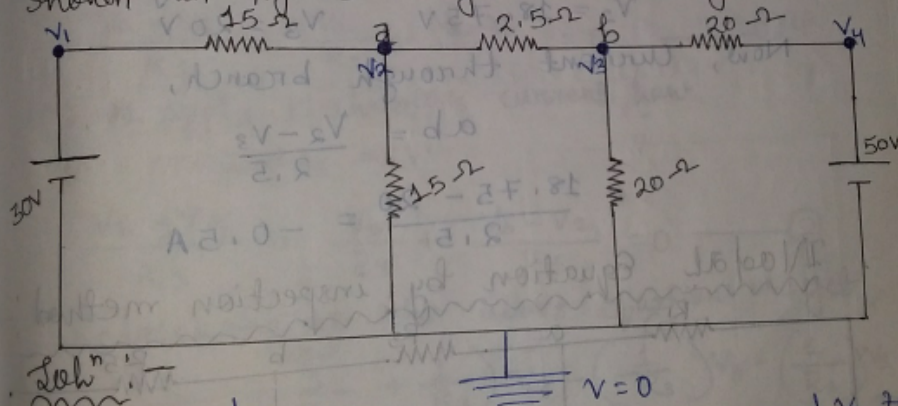Problem :-

Find current through branch ab of circuit shown in figure using nodal analysis.



Soln :-

5 node reference node $V=0$ and V_1, V_2, V_3 and V_4 to the non-reference nodes.

from fig : $V_1 - V = 30 \Rightarrow V_1 = 30V$

and $V_4 - V = 50 \Rightarrow V_4 = 50V$

Now applying KCL at node 2,

$$\frac{V_2 - V_1}{15} + \frac{V_2 - V_3}{2.5} + \frac{V_2 - V}{15} = 0$$

$$\Rightarrow V_2 - V_1 + 6(V_2 - V_3) + V_2 - V = 0$$

$$\Rightarrow V_2 - V_1 + 6V_2 - 6V_3 + V_2 = 0$$

$$\Rightarrow 8V_2 - 6V_3 = 30 \quad \text{--- (1)} \quad \boxed{V_1 = 30V}$$

Similarly applying KCL at node 3,

$$\frac{V_3 - V_2}{2.5} + \frac{V_3 - V_4}{20} + \frac{V_3 - V}{20} = 0$$

$$\Rightarrow 8(V_3 - V_2) + V_3 - V_4 + V_3 - V = 0$$

$$\Rightarrow \cancel{8V_3} - 8V_2 + V_3 - V_4 + V_3 = 0$$

$$\Rightarrow -8V_2 + 10V_3 = 50 \quad \text{--- (2)} \quad \boxed{V_4 = 50V}$$

Solving equⁿ (1) and (2), we get


$$V_2 = 18.75V, \quad V_3 = 20V$$

Now, current through branch,


$$ab = \frac{V_2 - V_3}{2.5}$$

$$= \frac{18.75 - 20}{2.5} = -0.5A$$

Nodal Equation by inspection method:-

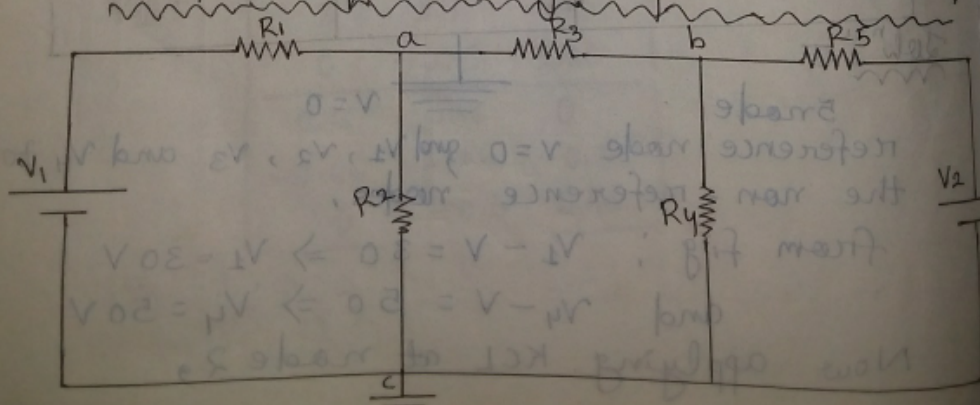

nodes = a, b
reference node = c

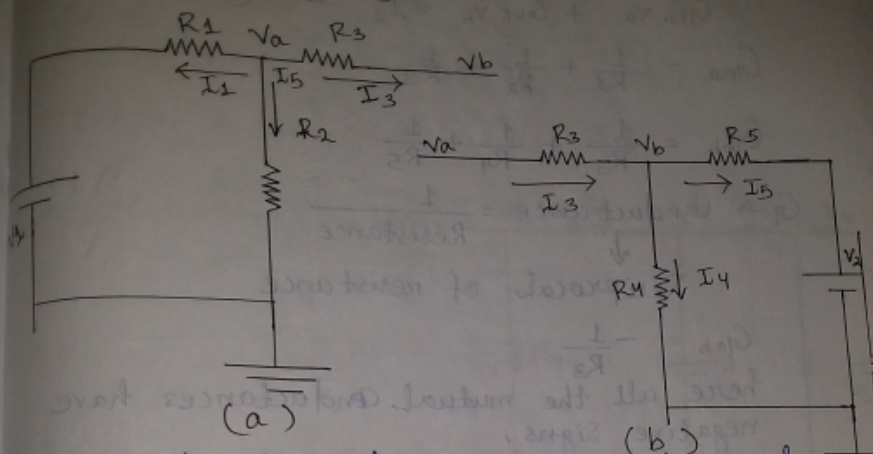

(a) According to Kirchhoff's current law we have =

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_a - V_1}{R_1} + \frac{V_a}{R_2} + \frac{V_a - V_b}{R_3} = 0 \quad \text{--- (1)}$$

(b) we apply Kirchhoff's current law

$$I_4 + I_5 = I_3$$

$$\frac{V_b - V_a}{R_3} + \frac{V_b}{R_4} + \frac{V_b - V_2}{R_5} = 0 \quad \text{--- (2)}$$

Rearranging the above equations we get

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_a - \left(\frac{1}{R_3} \right) V_b = \left(\frac{1}{R_1} \right) V_1 \quad \text{--- (3)}$$

$$\left(-\frac{1}{R_3} \right) V_a + \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) V_b = \frac{V_2}{R_5} \quad \text{--- (4)}$$

In general, the above equation can be written as

$$G_{aa} V_a + G_{ab} V_b = I_1 \quad \text{--- (5)}$$

$$G_{ba} V_a + G_{bb} V_b = I_2 \quad \text{--- (6)}$$

$$G_{aa} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$G_{bb} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$

$$G \rightarrow \text{Conductance} = \frac{1}{\text{Resistance}}$$

↓

Reciprocal of resistance


$$G_{ab} = -\frac{1}{R_3}$$

here all the mutual conductances have negative signs.

$$G_{ba} = -\frac{1}{R_3}$$

G_{aa} = Sum of self conductance of node 1.

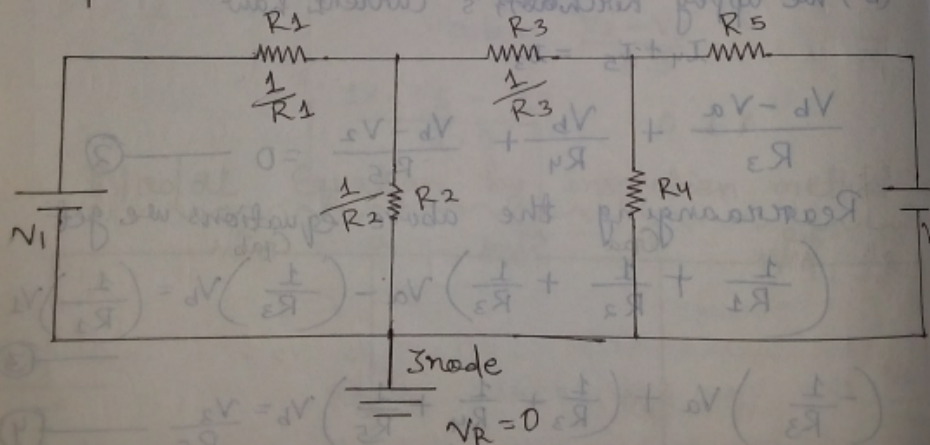G_{ab} = mutual conductance between node 1 and 2.



G_{ab} = mutual conductance between node 1 and 2. $\left(\frac{1}{R_3}\right)$


$$G_{ba} = \frac{1}{R_3}$$

$$G_{bb} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}$$

$$G_{11} V_1 \pm G_{12} V_2 \pm G_{13} V_3 = I_1$$

$$\pm G_{21} V_1 + G_{22} V_2 \pm G_{23} V_3 = I_2$$
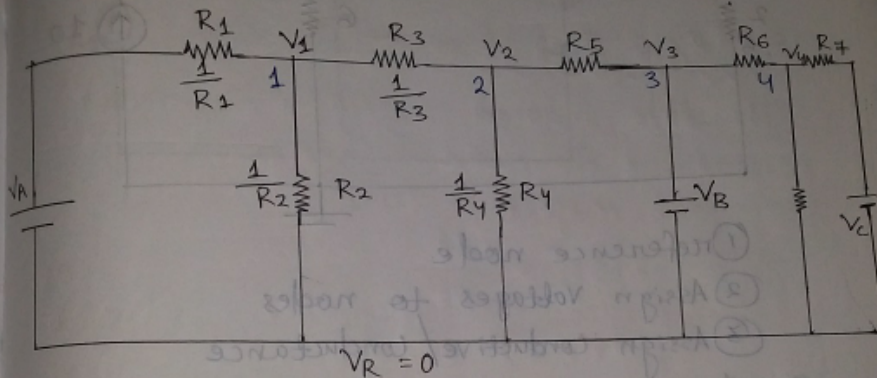
$$\pm G_{31} V_1 \pm G_{32} V_2 + G_{33} V_3 = I_3$$




$$G_{11} V_1 \pm G_{12} V_2 \pm G_{13} V_3 \pm G_{14} V_4 = I_1$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_1 \pm \frac{1}{R_3} V_2 + 0 + 0 = \frac{V_A}{R_2}$$

$$\pm G_{21} V_1 + G_{22} V_2 \pm G_{23} V_3 \pm G_{24} V_4 = I_2$$

$$\pm G_{31} V_1 \pm G_{32} V_2 \pm G_{33} V_3 \pm G_{34} V_4 = I_3$$
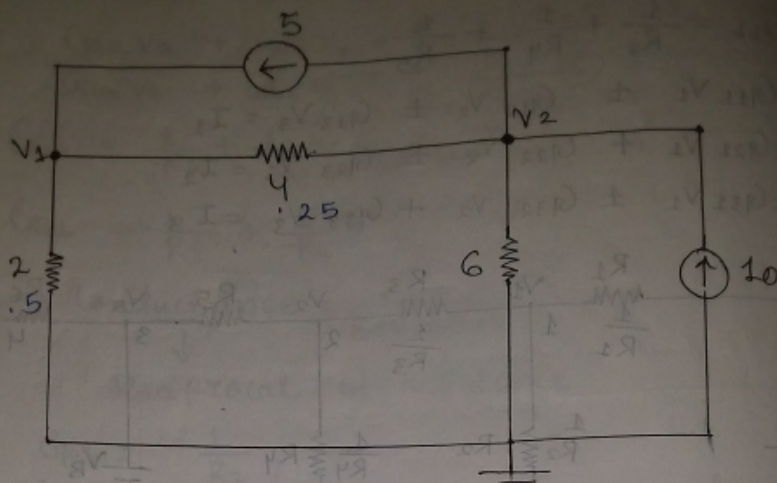
$$\pm G_{41} V_1 \pm G_{42} V_2 \pm G_{43} V_3 + G_{44} V_4 = I_4$$



- ① reference node
- ② Assign voltages to nodes
- ③ Assign conductive/conductance

$$G = \frac{1}{R}$$

Nodal analysis by inspection method

- ① Find a reference node with known voltage
- ② Assign voltages to other nodes
- ③ Assign conductance to each resistor
- ④ Find the elements of the conductance matrix
 - (a) For each node G_{ii}
 - (b) between each 2 nodes $G_{ij} = G_{ji}$
- ⑤ Set up the node Equations in matrix form
- ⑥ Solve the node-voltage Equations.